

Assignment 2

Ruizhi Zhang


8230108665

Link:


https://github.com/ruizhiz/-EE-599_Ruizhi_Zhang_8230108665.git

Barrel Shifter


The attached files include: tb.v, top.v, barrel_shifter.v, stage.v, shift.v. tb.v is used to do simulation test. barrel_shifter.v is our IP core. However, it has too many input and output pins, and cannot be implemented on FPGA directly. So, top.v is used to help to do implementation. So, only in implementation part, top.v is included in our schematics.

 

Picture 1: the overview of whole waveform

 

Picture 2: the first part of waveform

 

Picture 3: the second part of waveform

In our testbench, both input element a_in and shifter are generated by \$urandom.

As we can see from the waveform, the input elements a_in are:

4317_ceaa_4855_6cb5_5a1f_c7d2_37cc_0d2a, c1e9_4561_c4de_5de3_52bc_5c1c_a411_7b39, e60c_78a5_a729_16e2_9a52_a232_eae3_b6b6, e781_8ad2_e13e_1995_c4ad_0677_510d_dfa3, 6151_5afd_987b_451b_86d4_fa42_9c8a_73ce.

and the corresponding shifter are: e, e, 3, b, 0.


The outputs are:

0d2a_4317_ceaa_4855_6cb5_5a1f_c7d2_37cc, 7b39_c1e9_4561_c4de_5de3_52bc_5c1c_a411, a5a7_2916_e29a_52a2_32ea_e3b6_b6e6_0c78, 7751_0ddf_a3e7_818a_d2e1_3e19_95c4_ad06, 6151_5afd_987b_451b_86d4_fa42_9c8a_73ce.

That is what we expected. So, the result is right.


Part 1: 16 elements

1. Elaborated design

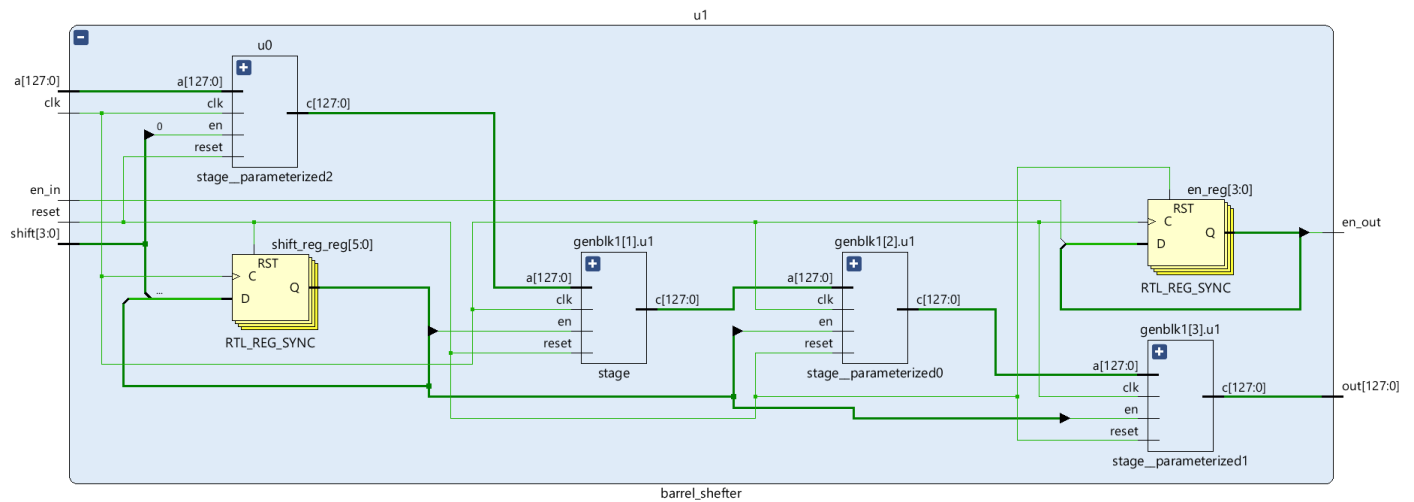


Picture 1: 16-element 8-bit barrel shifter

Barrel shifter includes 4 stage.

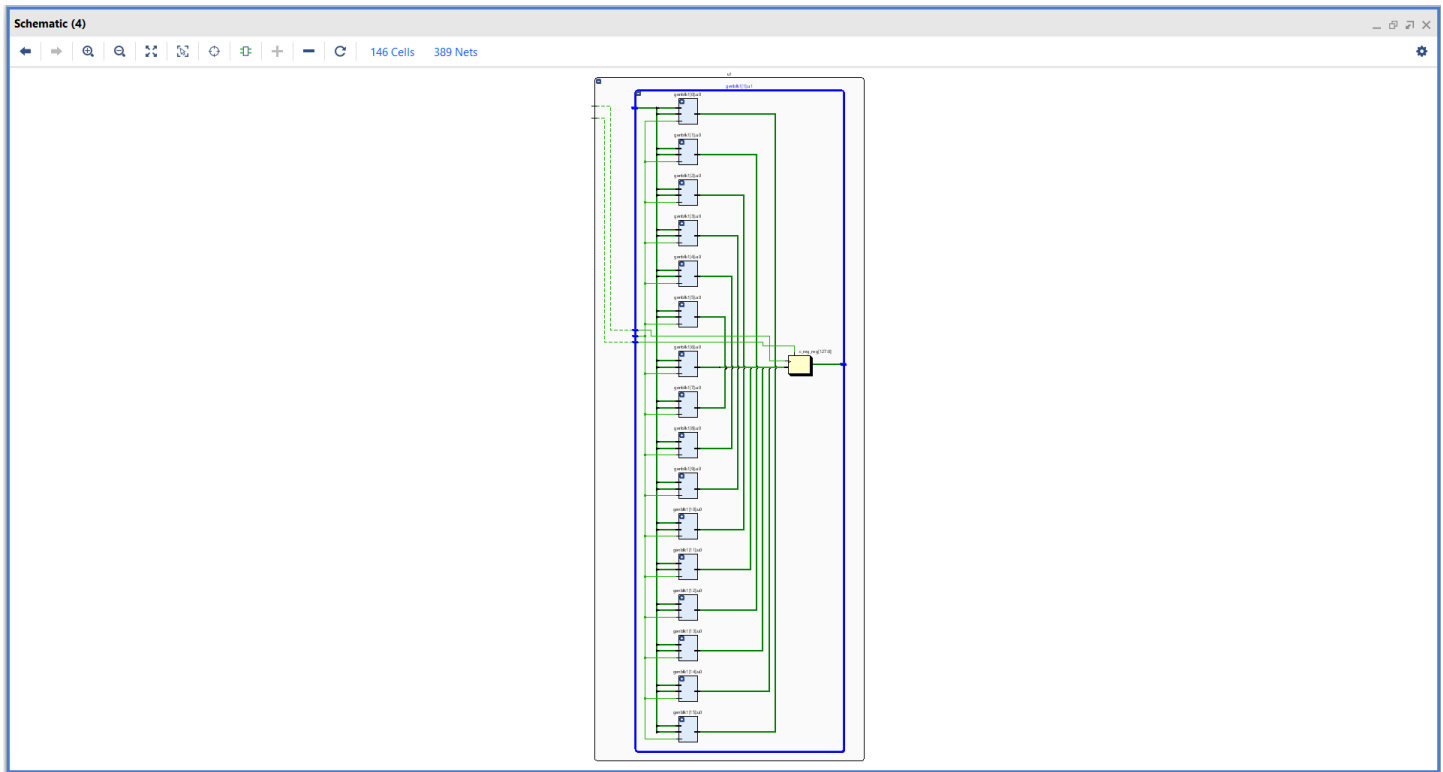


Picture 2: stage

1 stage include 16shifter and one 128-bit FF.

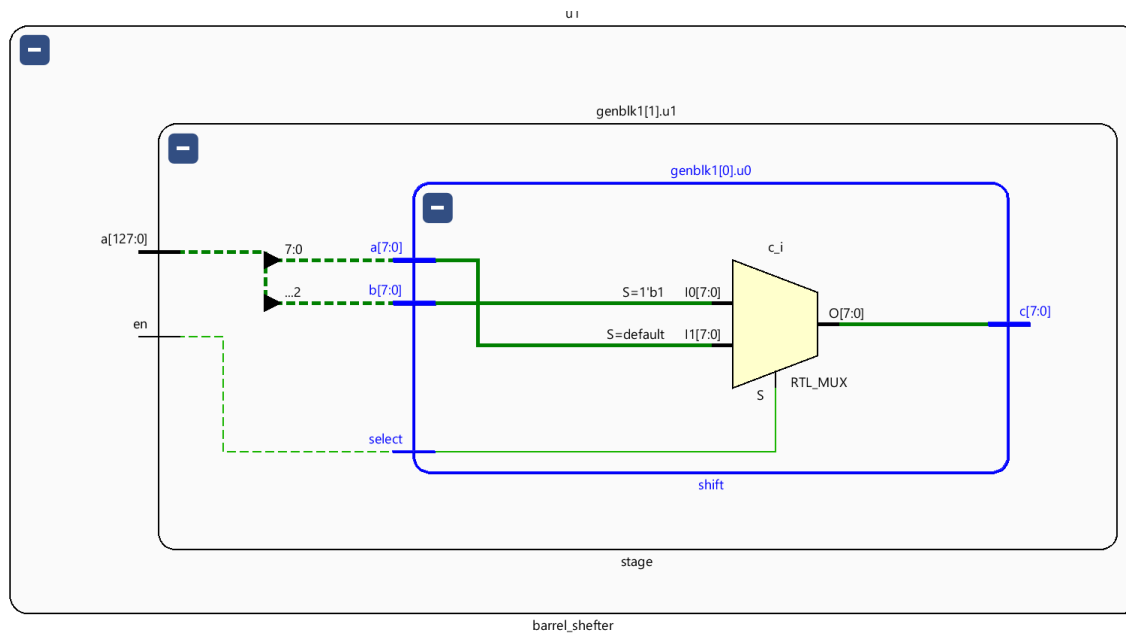


Picture 3: shifter unit

2. Synthesis and estimation

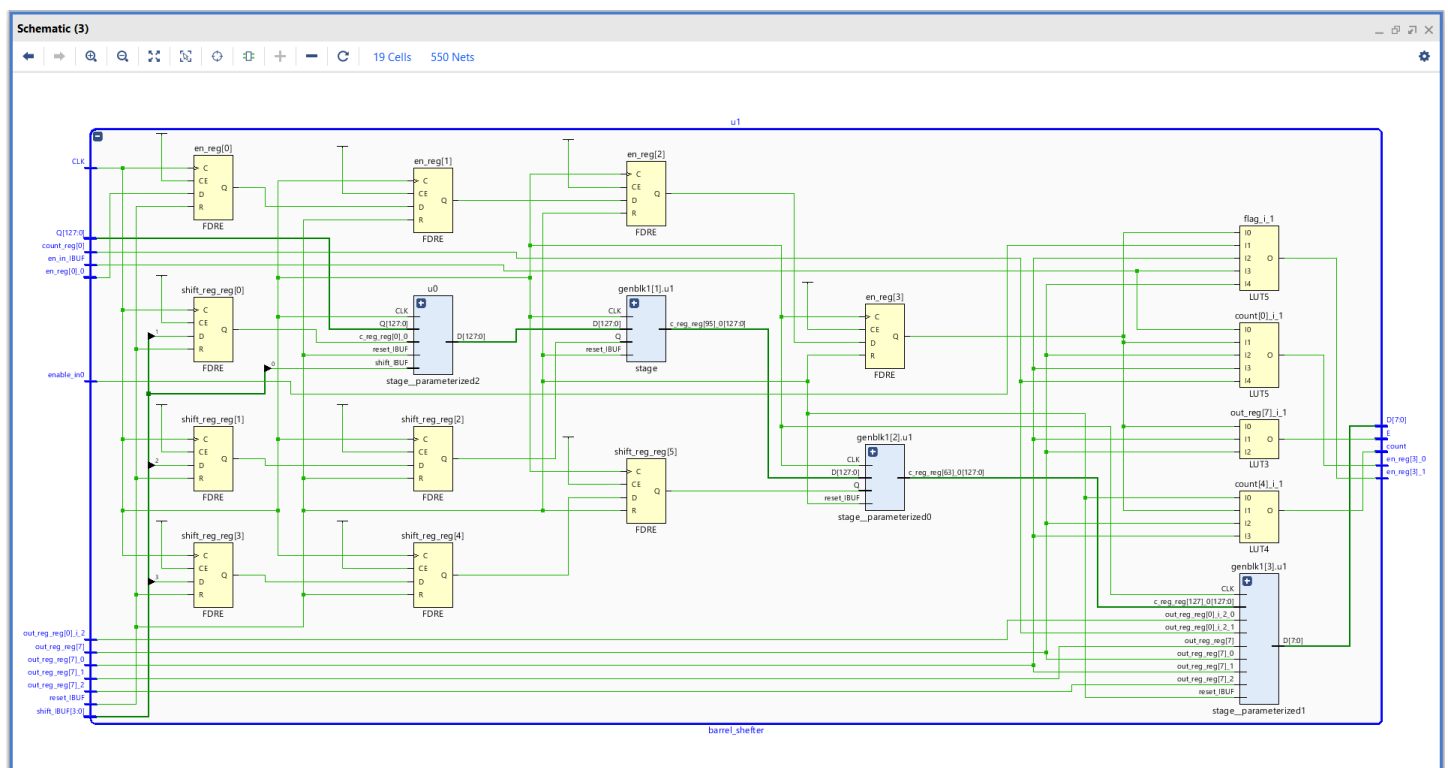

Picture 1: the synthesis schematic

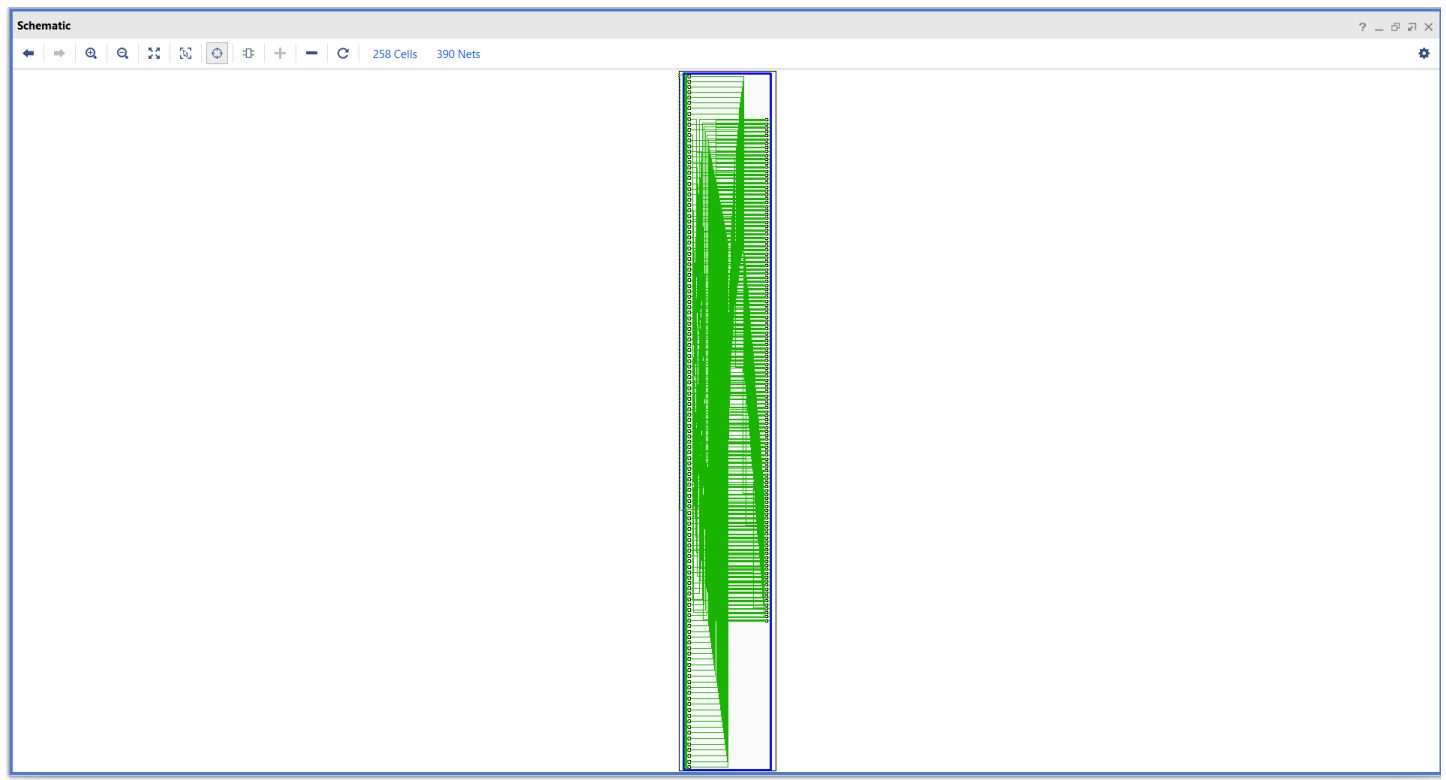

Picture 2: the schematics of single stage

Utilization			
		Post-Synthesis	Post-Implementation
Graph Table			
Resource	Utilization	Available	Utilization %
LUT	319	14400	2.22
FF	666	28800	2.31
IO	24	54	44.44
BUFG	1	32	3.13

Picture 3: resource estimation

Design Timing Summary


Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 5.607 ns	Worst Hold Slack (WHS): 0.156 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 679	Total Number of Endpoints: 679	Total Number of Endpoints: 667

All user specified timing constraints are met.

Picture 4: timing estimation


Part 2: 64 element barrel shifter

1. Elaborated design

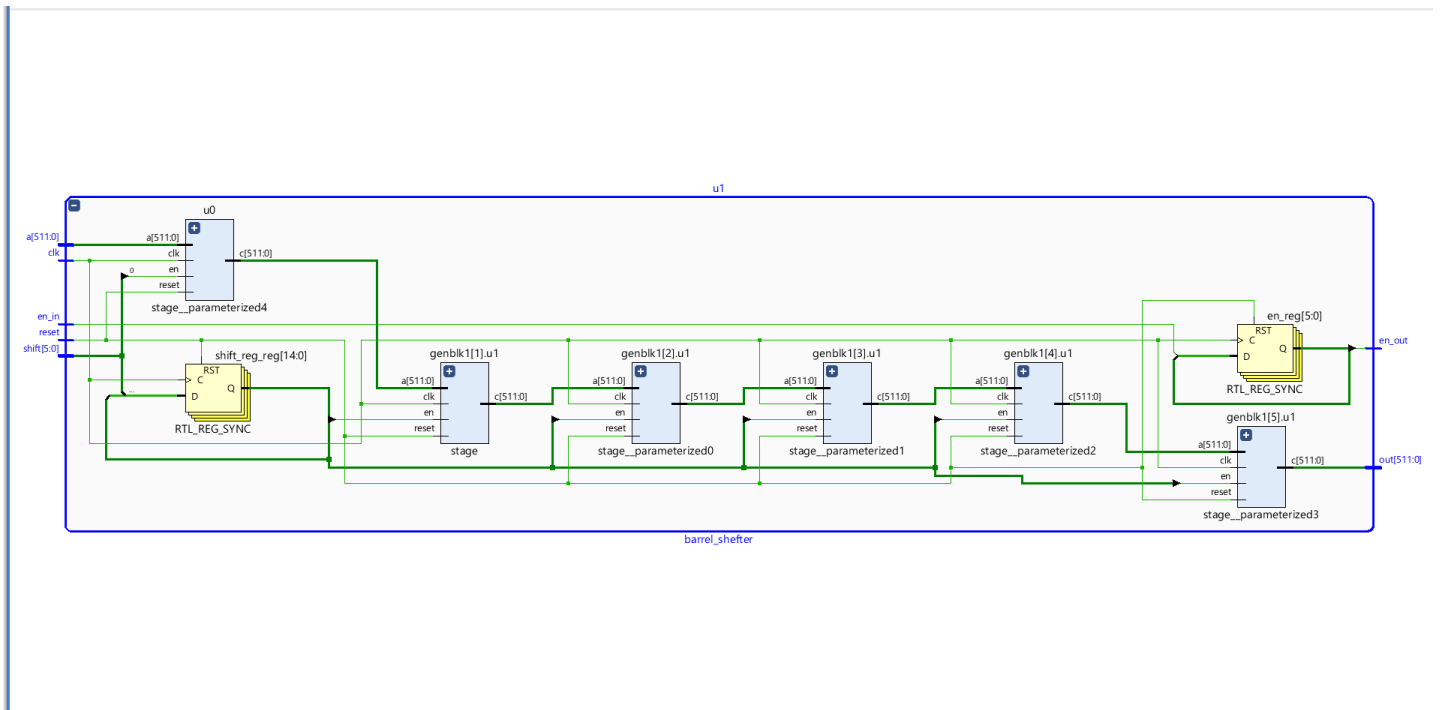


Picture 1: 64-element 8-bit barrel shifter

Barrel shifter includes 6 stage.

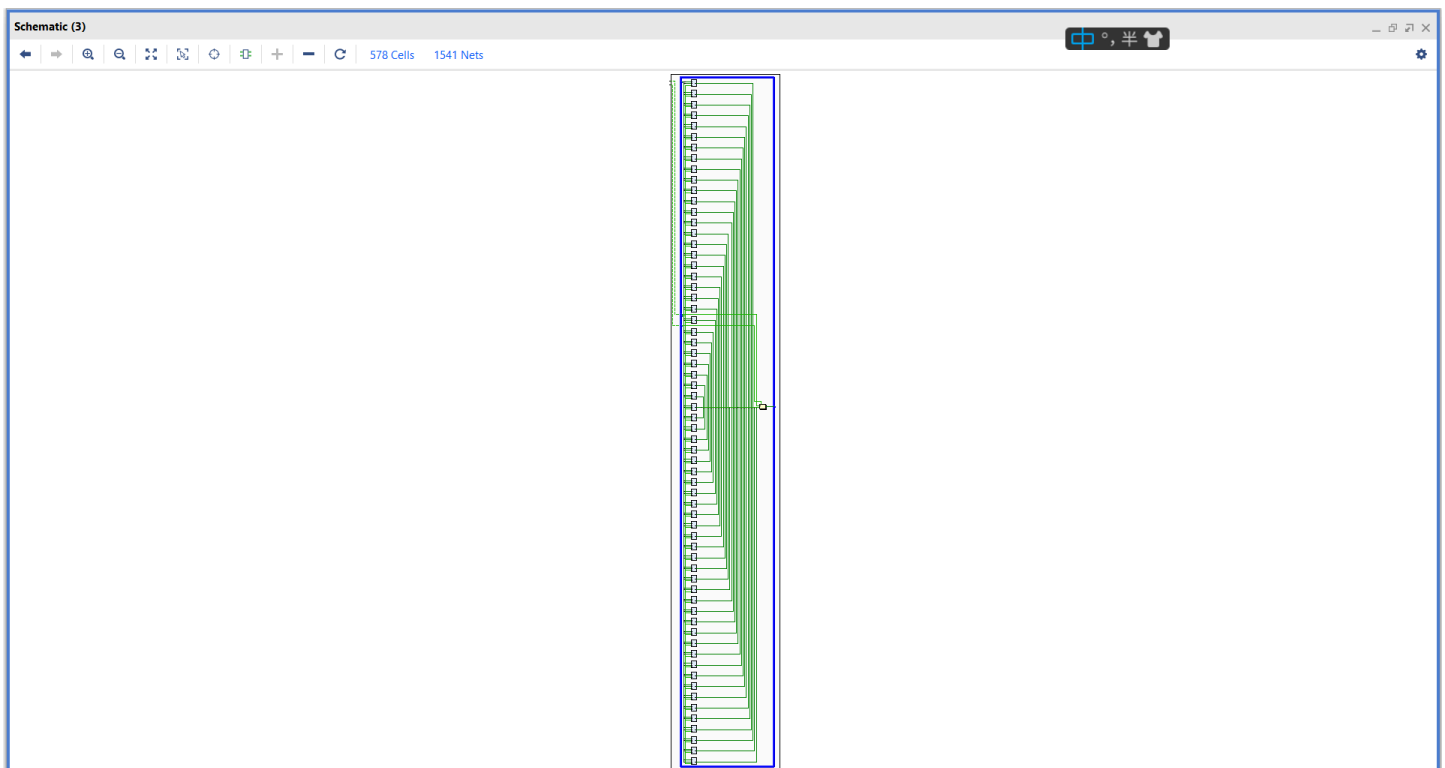


Picture 2: stage

1 stage include 64 shifters and one 512-bit FF.

 

Picture 3: shifter unit

2. Synthesis and estimation

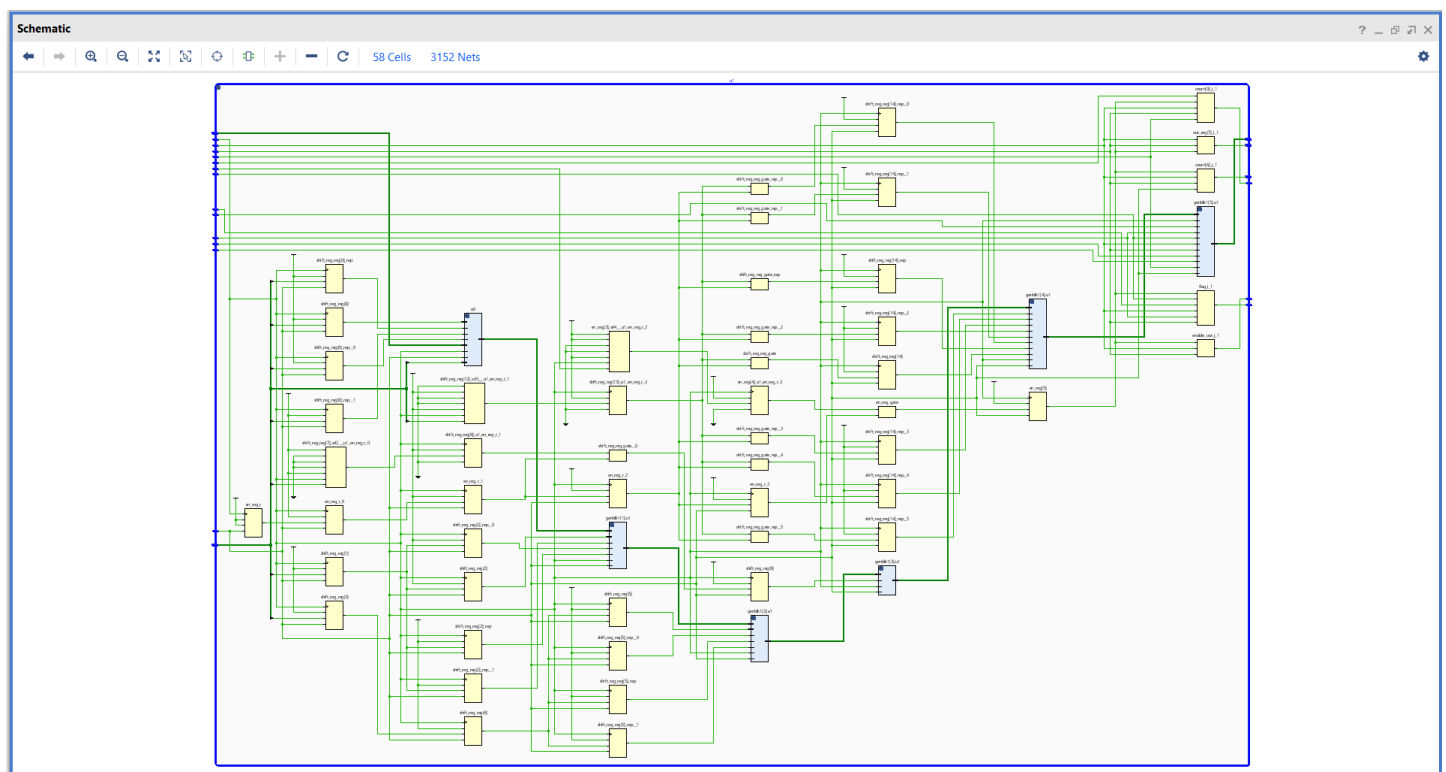

Picture 1: the synthesis schematic

Utilization			
		Post-Synthesis	Post-Implementation
Graph Table			
Resource	Utilization	Available	Utilization %
LUT	2023	14400	14.05
LUTRAM	3	6000	0.05
FF	3635	28800	12.62
IO	26	54	48.15
BUFG	1	32	3.13


Picture 2: resource estimation

Design Timing Summary			
Setup		Hold	Pulse Width
Worst Negative Slack (WNS): 3.976 ns		Worst Hold Slack (WHS): 0.043 ns	Worst Pulse Width Slack (WPWS): 4.146 ns
Total Negative Slack (TNS): 0.000 ns		Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0		Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 3649		Total Number of Endpoints: 3649	Total Number of Endpoints: 3639
All user specified timing constraints are met.			

Picture 3: timing estimation


systolic array

the attached file include: adder.v, multi.v, tb.v, top.v, unit.v. tb.v is used to do simulation test for 16 * 16 matrices. Top.v is systolic array. Unit.v is processing elements.

 


Picture 1: the overview of whole waveform


The out signal will output one row (16 elements) per cycle, and is valid when en_out is high.

 


Picture 2: the first part of waveform

 


Picture 3: the second part of waveform

 


Picture 4: the third part of waveform

 

Picture 5: the fourth part of waveform

 


Picture 6: part 5 of the waveform

 


Picture 7: part 6 of the waveform


The above are input signals. The following are output signals.

 


Picture 8: part 1 of output waveform

 

Picture 9: part 2 of output waveform

 

Picture 10: part 3 of output waveform

 


Picture 11: part 4 of output waveform

Based on the waveform, we could know our circuits is correct.


Part 1: 16 * 16 elements

1. Elaborate design

 


Picture 1: schematics of Systolic array

It includes 16*16 PEs.

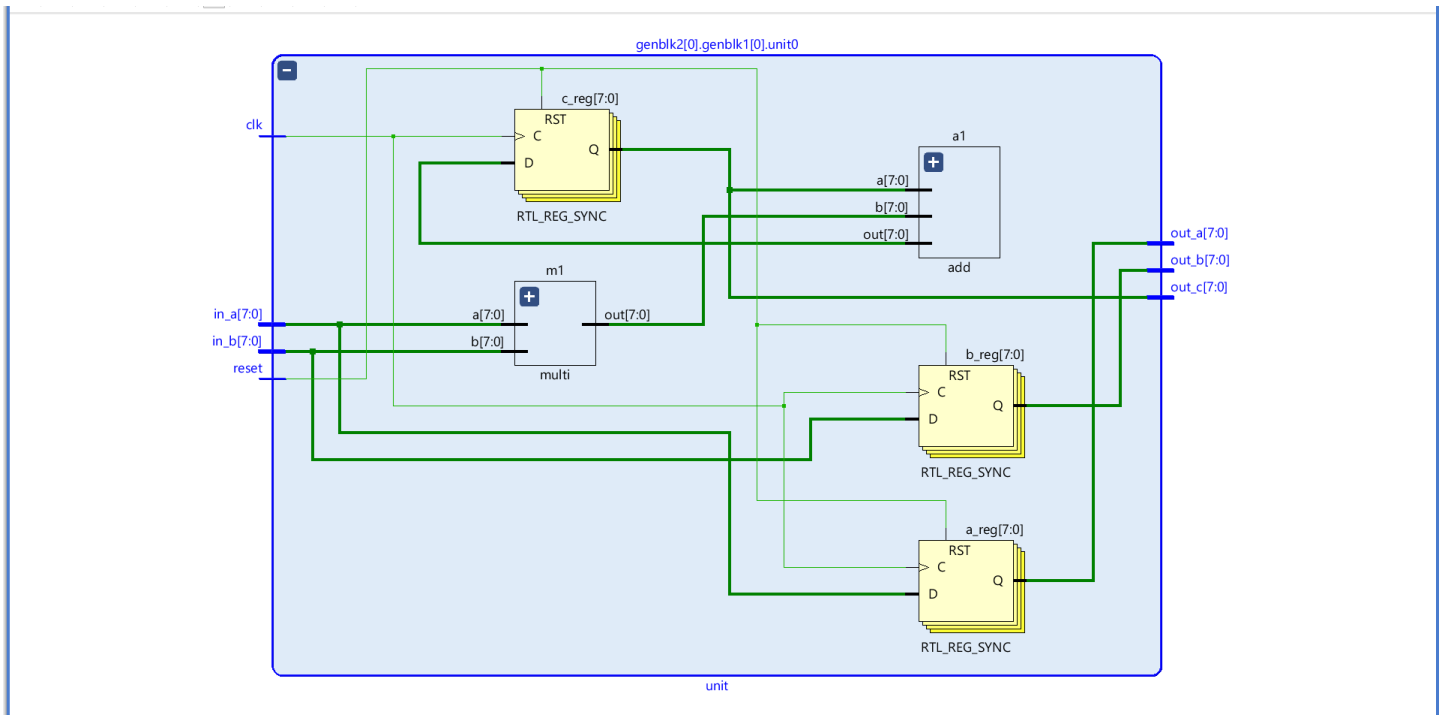


Picture 2: schematics of PE

It includes 1 adder and 1 multiply module.

 


Picture 3: adder module

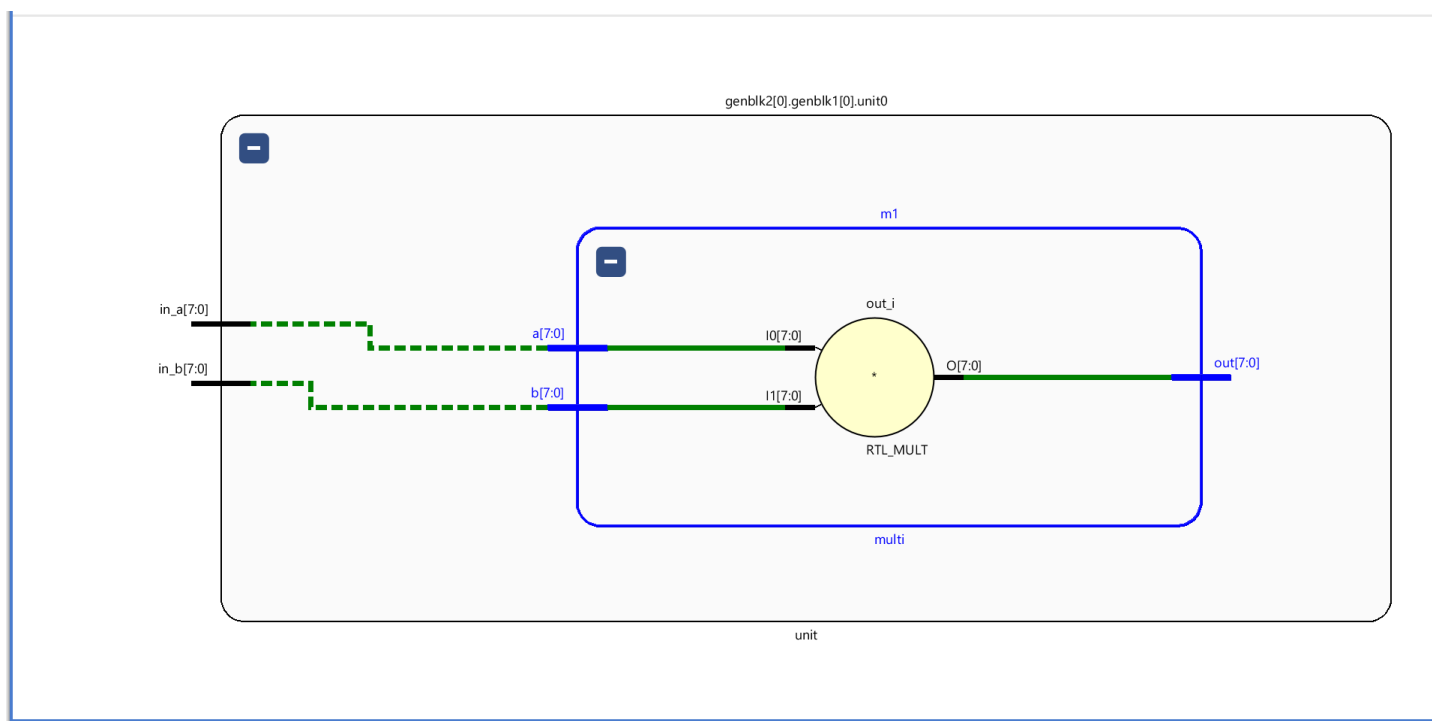


Picture 4: multiply module


2. Synthesis design

 


Picture 1: the schematics of whole design

 

Picture 2: the synthesized schematics of PE

 

Picture 3: the schematics of multiply module

 

Picture 4: the schematics of adder module

3. Estimation

Utilization			
		Post-Synthesis	Post-Implementation
Graph Table			
Resource	Utilization	Available	Utilization %
LUT	10735	14400	74.55
FF	6233	28800	21.64
IO	28	54	51.85
BUFG	1	32	3.13

Picture 1: resource estimation

Power		Summary	On-Chip
Total On-Chip Power:		0.189 W	
Junction Temperature:		27.2 °C	
Thermal Margin:		57.8 °C (4.9 W)	
Effective θ /A:		11.5 °C/W	
Power supplied to off-chip devices:		0 W	
Confidence level:		Low	
Implemented Power Report			

Picture 2: power estimation

Design Timing Summary


Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 4.151 ns	Worst Hold Slack (WHS): 0.061 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 6282	Total Number of Endpoints: 6282	Total Number of Endpoints: 6234

All user specified timing constraints are met.

Picture 3: timing estimation


Part 1: 32 * 32 elements

1. Elaborate design

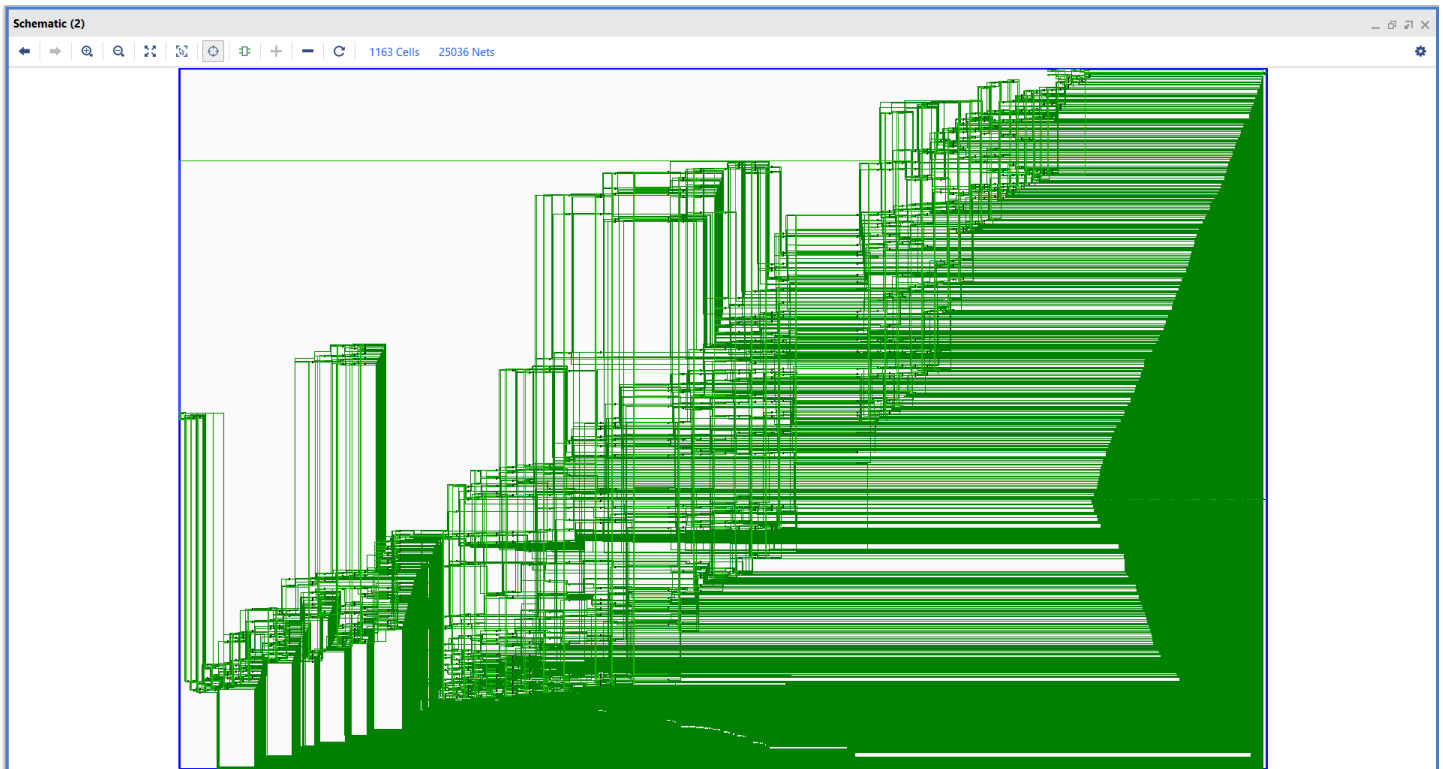


Picture 1: schematics of Systolic array

It includes 32*32 PEs.

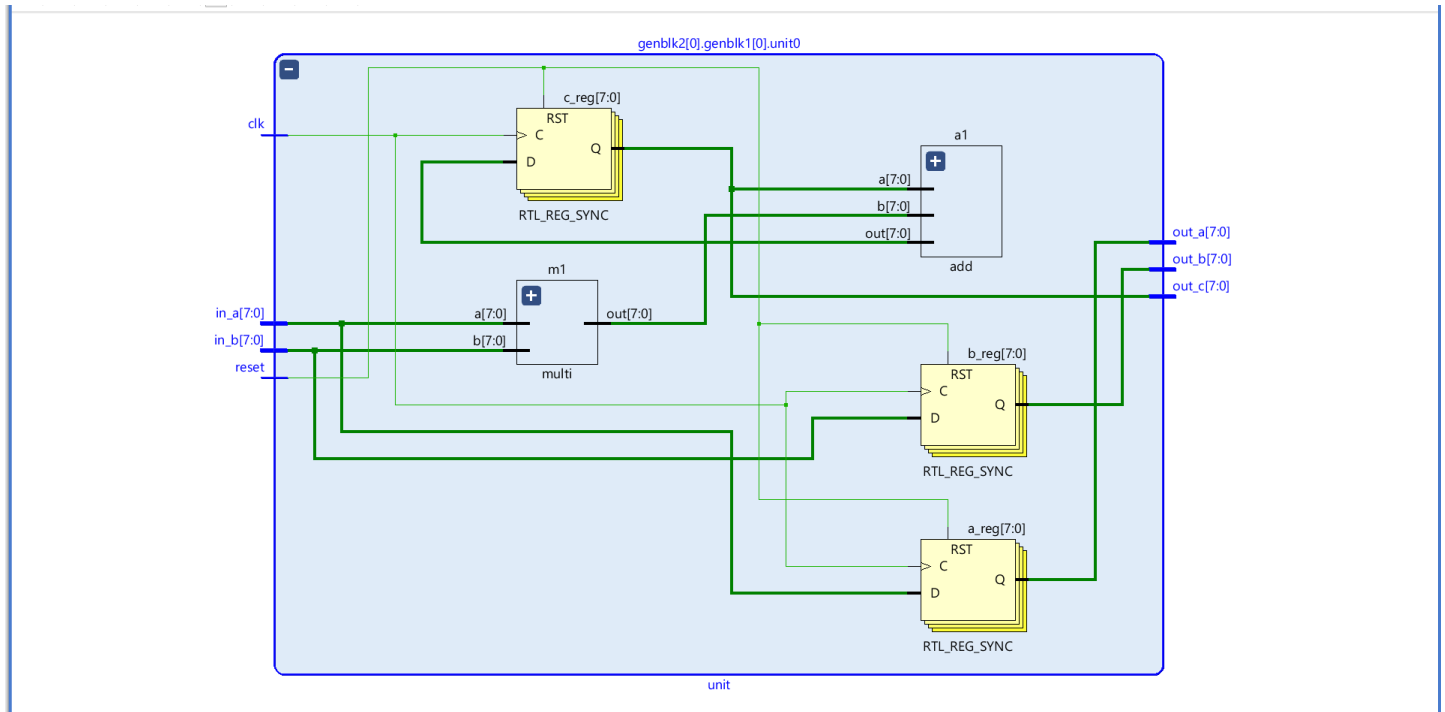


Picture 2: schematics of PE

It includes 1 adder and 1 multiply module.

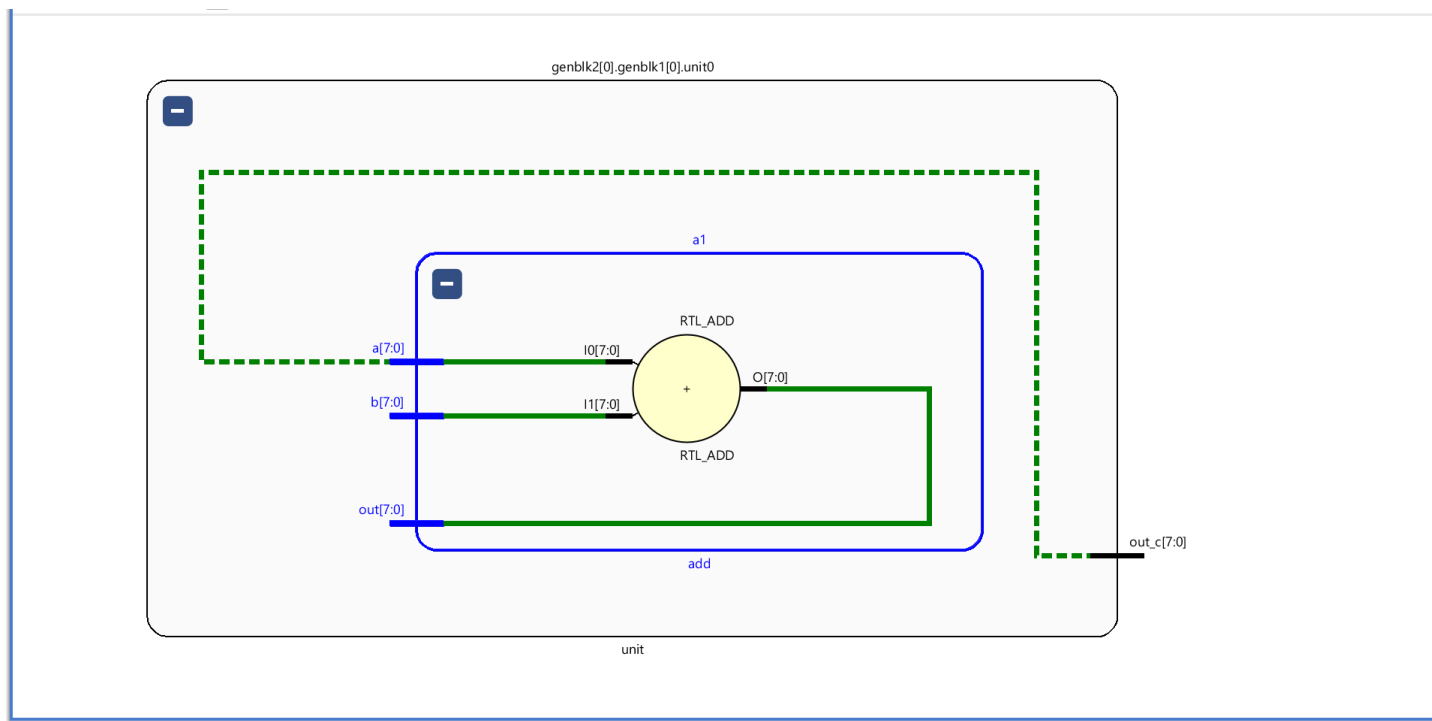

Picture 3: adder module

 


Picture 4: multiply module


2. Synthesis design




Picture 1: the schematics of whole design

 

Picture 2: the synthesized schematics of PE

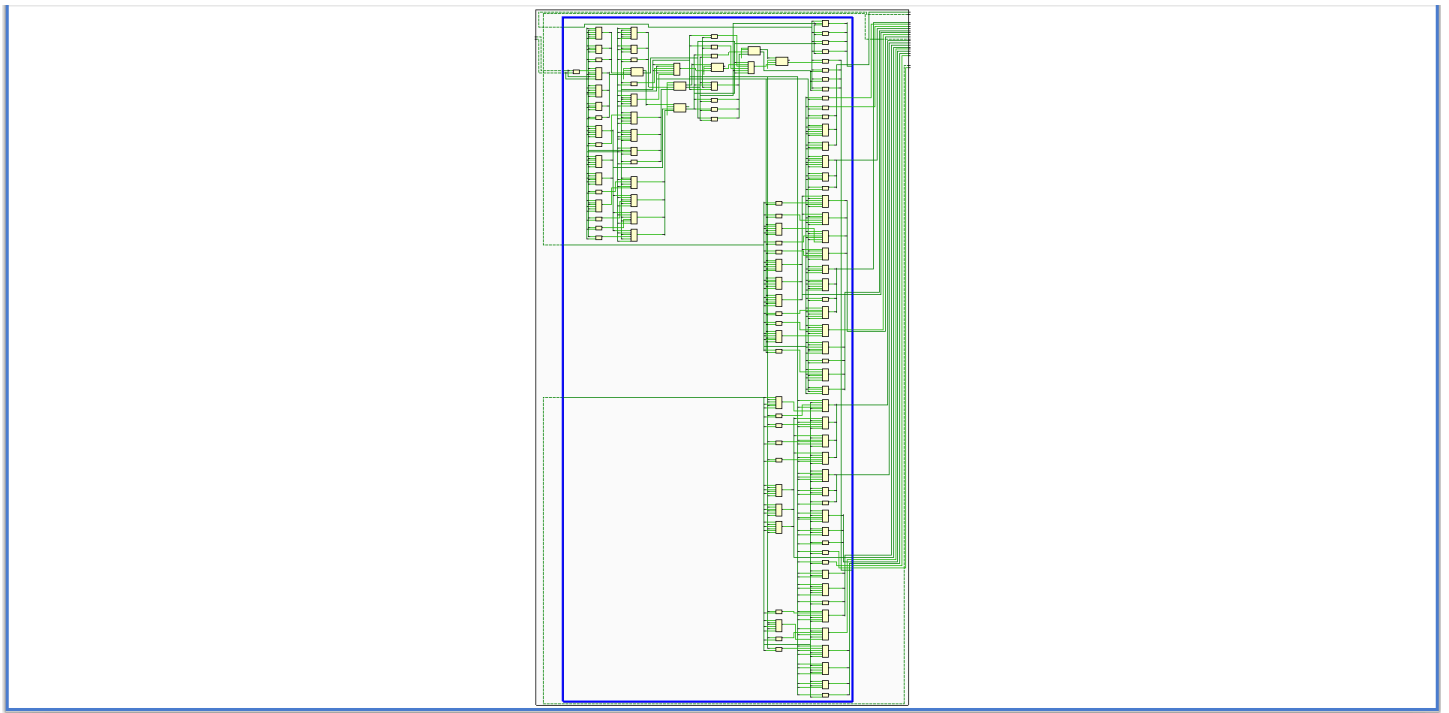

Picture 3: the schematics of multiply module

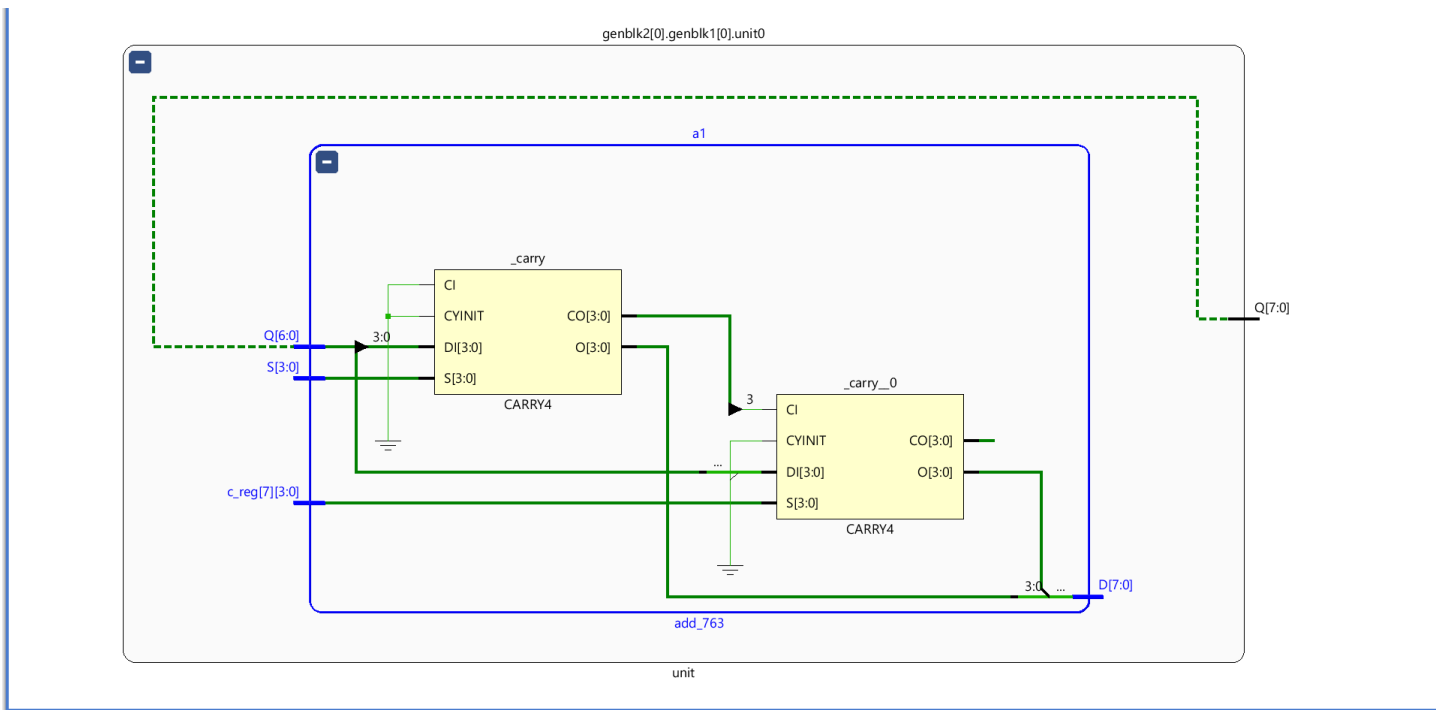

Picture 4: the schematics of adder module

3. Estimation

Utilization				Post-Synthesis Post-Implementation	
				Graph	Table
Resource	Estimation	Available	Utilization %		
LUT	46686	14400	324.21		
FF	24799	28800	86.11		
IO	28	54	51.85		
BUFG	1	32	3.13		

Picture 1: resource estimation

Because the circuit has over-utilized the FPGA resource, the implementation is failed, so, there is no power or timing estimation.